

CDPD Solutions From CML

Cellular Digital Packet Data (CDPD) is a packet data transfer system currently employed to provide a digital data facility to run in parallel with the existing analogue AMPS cellular radiophone system using current frequencies and RF infrastructure.

Reusing AMPS infrastructure provides the CDPD system and therefore its participants with the same, wide geographical coverage as the cellphone voice network. CDPD supports such common protocols as TCP/IP and OSI/CLNP.

CDPD based digital communications is becoming increasingly popular for such varied applications as: 'The Mobile Office' (providing voice, Fax and data comms), Stock Control, Reporting and Audit, 'Swipe' Terminals, Telemetry, Fleet Control, Taxi and Courier Services, Electronic-Mail, Database Access, Hand-Held and Laptop Communications and Emergency and Security Services.

Equipments developed so far include: Cellular Telephones with integral Data Terminals, Stand-Alone Data Terminal Accessories, Personal Digital Assistants (PDA) and PCMCIA Radio Modem Cards for PCs and Laptops and Custom Radio Modems.

Consumer Microcircuits Limited offers microcircuits that can offer versatility, high performance and high savings in many CDPD peripherals.

Base Station or Mobile End Station (MES) Design Example

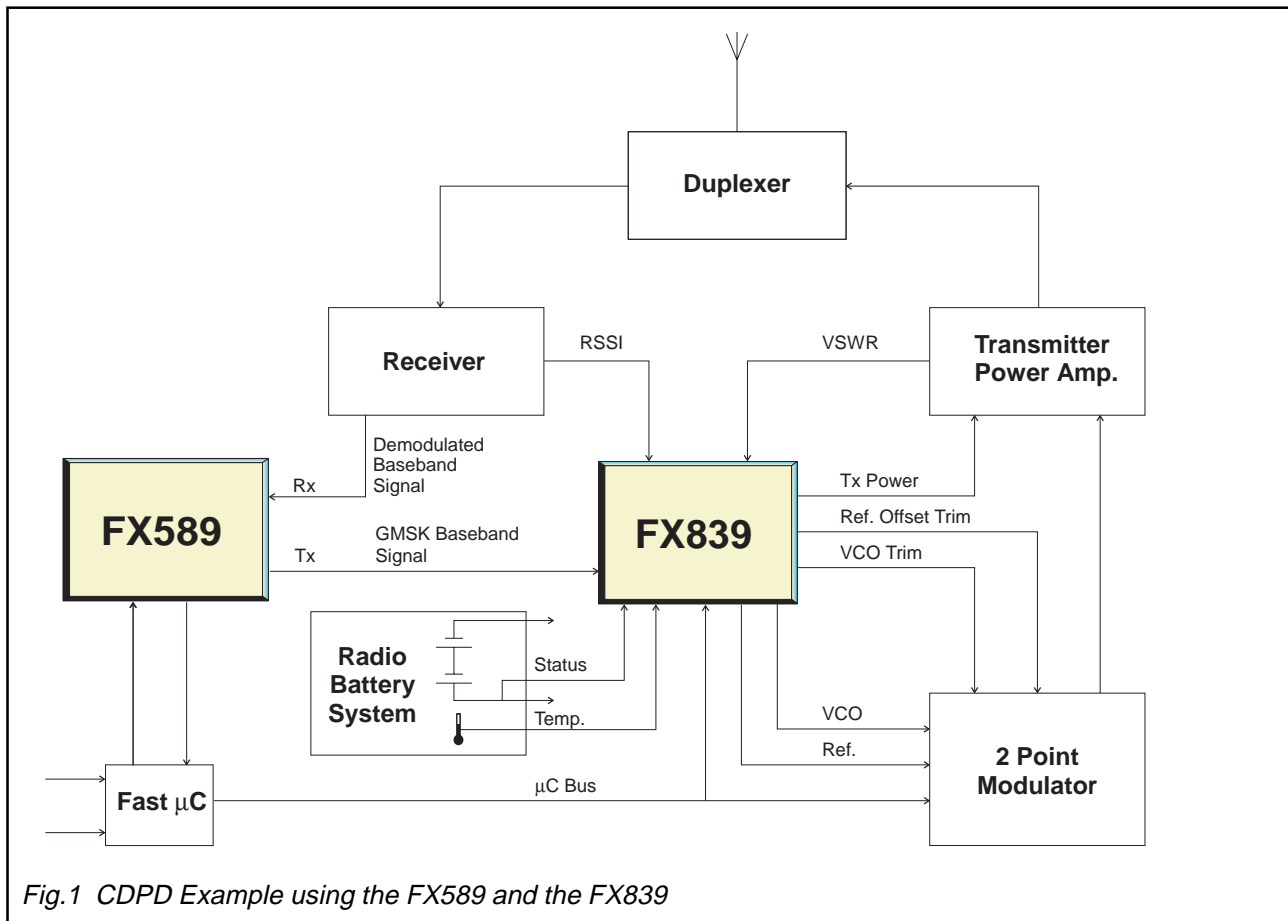


Fig.1 CDPD Example using the FX589 and the FX839

Mobile End Station (MES) Design Example - Optimised for low power operation

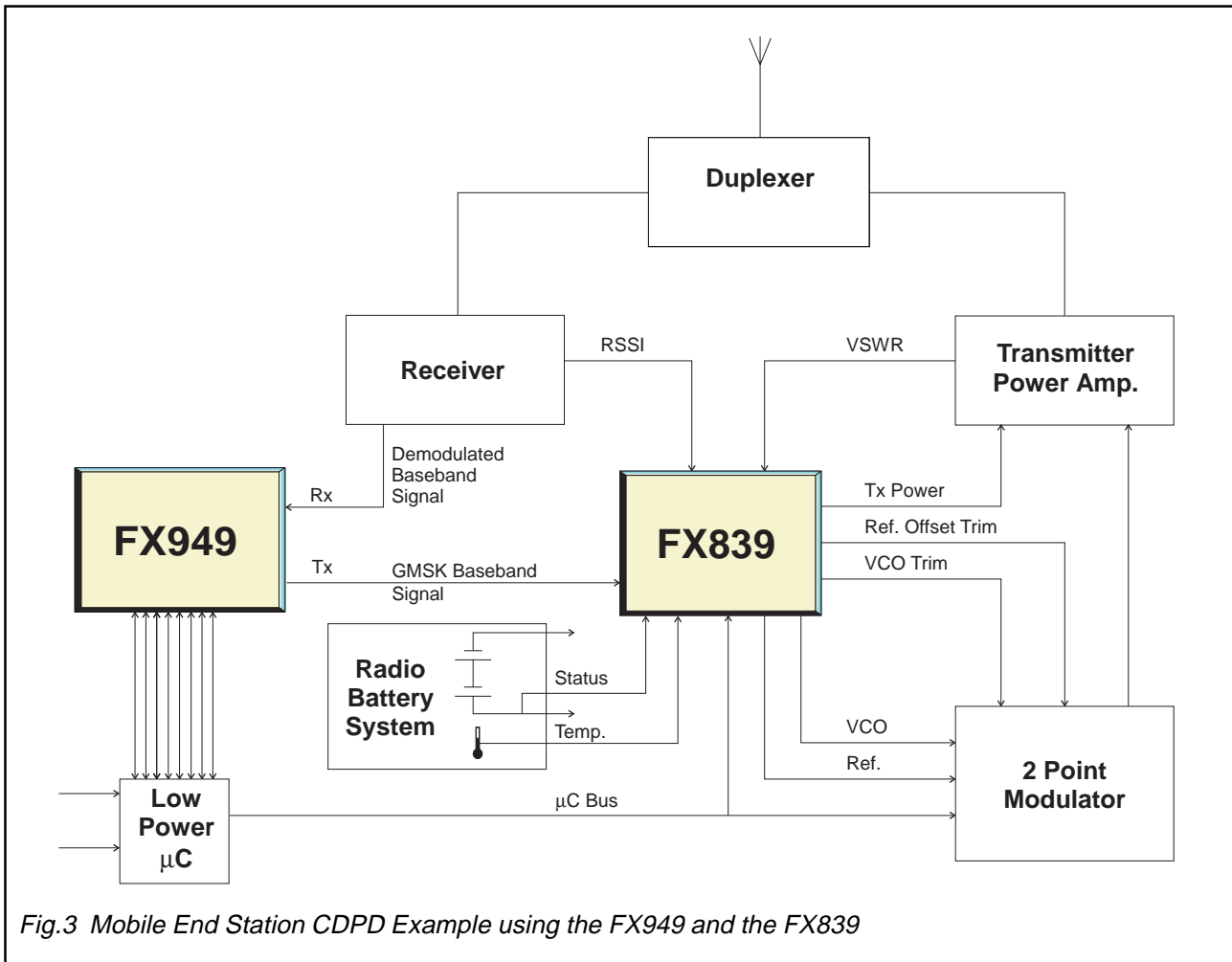


Fig.3 Mobile End Station CDPD Example using the FX949 and the FX839

The key to this successful low power MES design is the use of the FX949 CDPD formatted GMSK modem. The FX949, by using hardware to format data for transmission and to decode incoming data, significantly reduces the demands placed on the host µC. This allows the selection of a low speed, low power µC.

As in our first design example, the FX839 Analogue Control Interface is used to further reduce the demands on the µC, power budget and board space, as it carries out all necessary modulator control attenuation, DAC, ADC tasks.

The facility for IRQ generation on the FX839, can be used to achieve truly useful power savings by allowing the µC to sleep until one of the monitored inputs to one of the FX839's ADCs exceeds its pre-set threshold and generates an IRQ waking up the µC.

The FX949/FX839 combination offers power savings untouchable by the current generation of DSP alternatives.

Circuit Diagram:

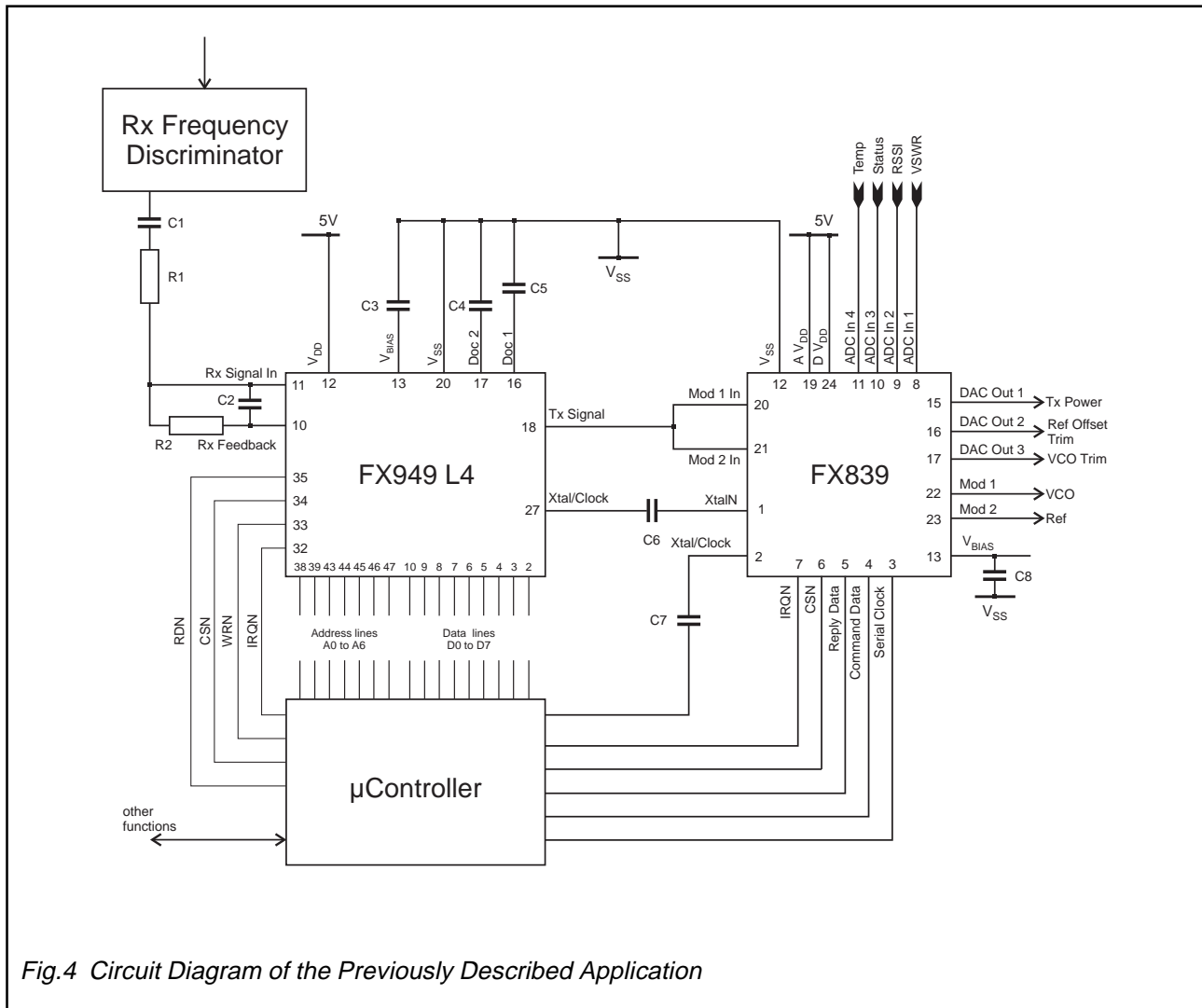


Fig.4 Circuit Diagram of the Previously Described Application

Mobile End Station (MES) Design Figure 4, Components List

Component	Value	Tol/Remarks			
R1	note 1		C1	note 1	
R2	100kΩ	±10%	C2	100pF	±20%
			C3	1.0μF	±20%
			C4	6.8nF	±20%
			C5	6.8nF	±20%
			C6	10pF	
			C7	10pF	
			C8	1.0μF	±20%

Notes

1. R1, R2, C1 and C2 form the gain components for the Rx Input. C1 and R1 should be chosen as required by the signal input level, using the following formula:

$$- R2/R1$$

Please note that diagrams contained within this document are outline schematics only; they are intended to show how CML products may be used. This Application Note is intended to be used in conjunction with the current CML Product Data Sheet; printed Specifications apply. CML does not assume any responsibility for the use of any circuitry described. No circuit patent licences are implied and CML reserves the right at any time without notice to change the said circuitry.